

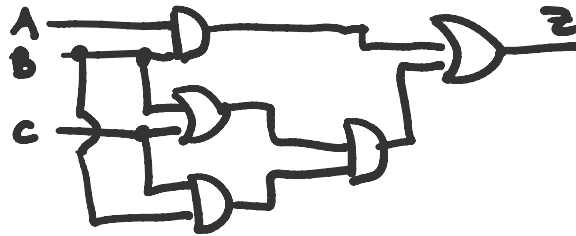


Worked Example - Simplifying Circuits


1. Simplify this circuit:

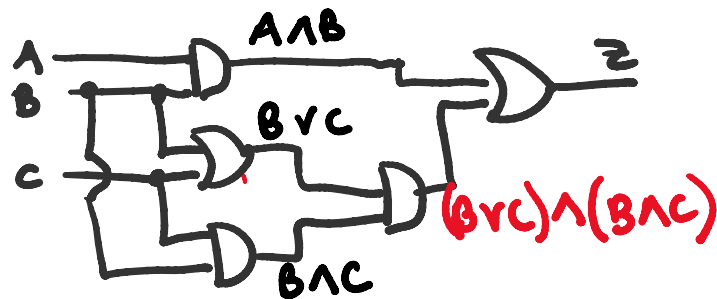

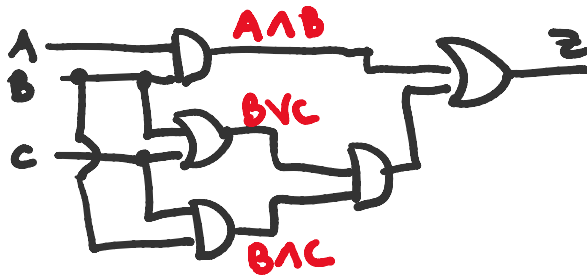2. Write intermediate expressions for the output of each gate beginning from the left-hand side...



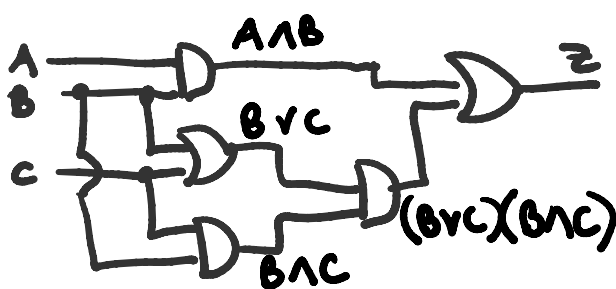3. Until you finally have an expression for the output (traditionally, the output is Q or Z but could be any letter).



$$Z = (A \wedge B) \vee [(B \vee C) \wedge (B \wedge C)]$$

4. At this point, you can use the laws of Boolean algebra to simplify:

$$(A \wedge B) \vee [(B \vee C) \wedge (B \wedge C)]$$

$$(A \wedge B) \vee [(B \wedge C) \wedge B) \vee (B \wedge C) \wedge C]$$

$$(A \wedge B) \vee [(B \wedge B) \wedge C) \vee (B \wedge (C \wedge C))]$$

$$(A \wedge B) \vee [(B \wedge C) \vee (B \wedge C)]$$

$$(A \wedge B) \vee (B \wedge C)$$

$$B \wedge (A \vee C)$$

Distributive

Associative (+ Commutative)

Idempotent

Idempotent again

Distributive

5. Redraw the new (simplified) circuit

